



LAB 1: De Morgan's Law

Pre lab: $(xy)' = \overline{xy} \rightarrow \overline{x+y} \rightarrow \text{truth table}$
 $(x+y)' = \overline{x+y} \rightarrow \overline{xy} \rightarrow \text{truth table}$

x	y	xy	$(xy)'$
1	1	0	0
1	0	1	1
0	1	1	1
0	0	1	1

truth table:

x	y	$(xy)'$	$\overline{xy}$
1	1	0	0
1	0	0	0
0	1	0	0
0	0	1	1

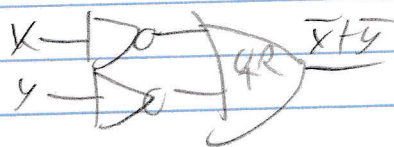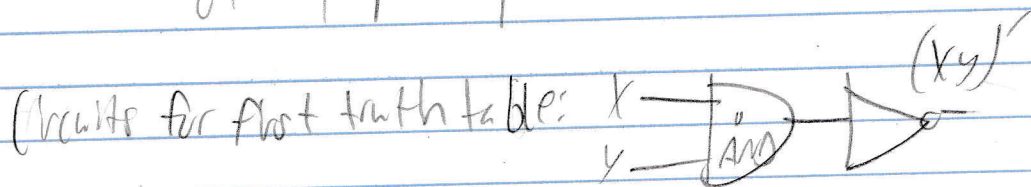

Circuit for second truth table:

